

Question 1 is COMPULSORY

Question 1

- (a) Convert $6.8 \times 10^{-5} \text{ W}$ to the closest standard metric prefix. **[2 marks]**
- (b) Convert 4.7 mA to amperes. **[2 marks]**
- (c) What is the rate of flow of free electrons in a conductive material called? **[2 marks]**
- (d) What is the opposition to current called? **[1 marks]**
- (e) To measure current with an ammeter, how would one connect the ammeter in a circuit? **[2 marks]**
- (f) For the circuit of Figure 1.1, calculate (i) the total resistance R_T and (ii) the values of the currents I_S , I_1 and I_2 . **[5 marks]**

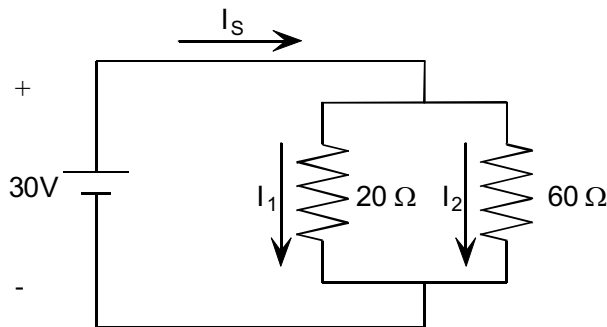


Figure 1.1

- (g) What is the relationship between the power rating of a resistor and its surface area? **[2 marks]**
- (h) For a circuit that contains a 50 V power supply and a 100Ω resistor, what power rating should be assigned to the resistor? **[3 marks]**
- (i) You got a bargain on a car media player at a flea market. When you got home, you discovered that it has a 6 V power supply that needs to draw 500 mA. However, your car has a 12 V system. You need a resistor that will drop 6 V at 500 mA. What value resistor do you need? **[3 marks]**
- (j) A smartphone uses a small 3.6 V lithium-ion battery with a nominal stored energy of 40 kJ. For how long will it power the phone if it draws (i) 100 mA of current when making a call and (ii) 200 mA when making a video call? **[4 marks]**
- (k) If a unit of electricity (1 kWh) costs 40 cents, how much will it cost to operate a 2400 W heater and twenty 10 W LED bulbs from 6:30 to 8:30 in the morning for a full week, and how many joules will be used? **[4 marks]**

[30 marks in total]

Answer any TWO questions from Questions 2, 3 and 4

Question 2

(a) State the following formulae:

(i) Kirchhoff's Current Law

[2 marks]

(ii) Kirchhoff's Voltage Law

[2 marks]

(iii) The Voltage Divider Rule

[2 marks]

(iv) The Current Divider Rule

[2 marks]

(b) The ammeter in the circuit of Figure 2.1 registers a value of 2A. Using this information, determine the value of the unknown resistor R. Proceed to calculate the power dissipated in this resistor. **[5 marks]**

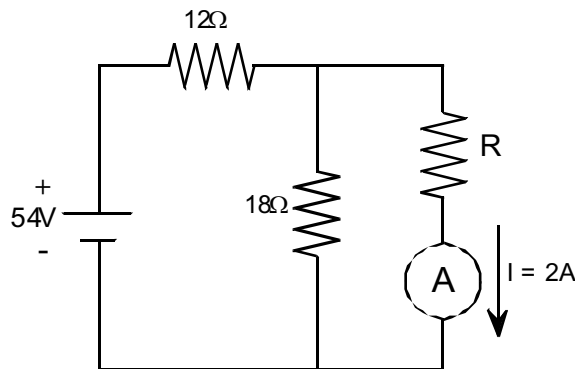


Figure 2.1

(c) For the circuit shown in Figure 2.2, use Kirchhoff's laws to calculate:

(i) The current I_1

[2 marks]

(ii) The current I_2

[2 marks]

(iii) The current I_3

[2 marks]

(iv) The voltage across the 45Ω resistor

[1 mark]

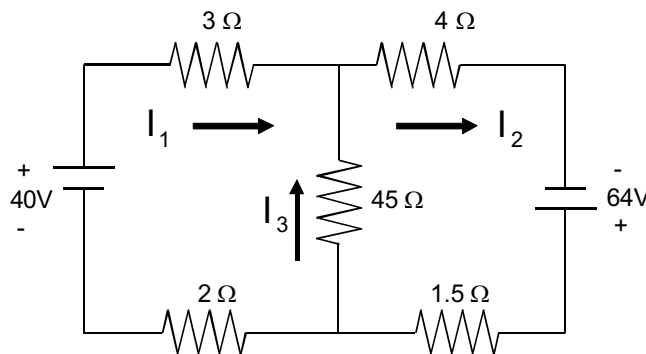


Figure 2.2

[20 marks total]

Question 3

- (a) For the circuit shown in Figure 3.1, with $V_s = 5\text{ V}$, calculate the total resistance for the circuit, the total current flowing out of the voltage source, and the individual currents flowing through R_1 , R_2 and R_3 . Repeat the calculations for $V_s = 10\text{ V}$. **[10 marks]**

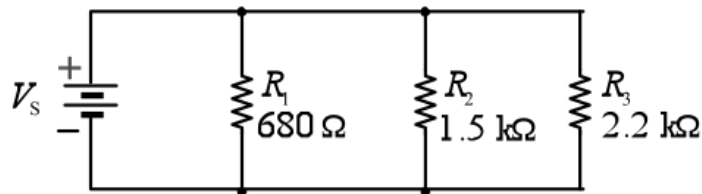


Figure 3.1

- (b) A standard 12 V battery in a car is used to power four identical interior lamps in parallel, as depicted in Figure 3.2. Assume that each lamp has a resistance of $192\ \Omega$. Explain what effects each of the following two scenarios will have on the voltage, current and resistance in the overall circuit *and* in the circuit elements in each of the branches:

- The conducting path through the first lamp is broken when the lamp bulb blows, **[3 marks]**
- A fifth path is added through a new lamp connected in parallel with the others. **[2 marks]**

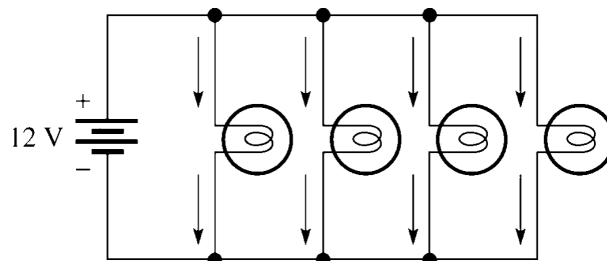


Figure 1.2

- (c) For the circuit of Figure 3.3, a voltmeter placed across either of the two resistors will show a voltage of 4.47 V. Explain what is happening. **[5 marks]**

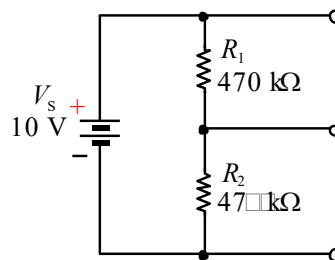


Figure 3.3

[20 marks in total]

Question 4

- (a) Assume a sinusoidal input voltage of $V_1 = 30 \text{ V}$ (peak) is connected across two resistors in series, R_1 and R_2 , both with a value of 1 k . Find (i) the RMS current flowing through resistor R_1 , and find (ii) the RMS voltage across resistor R_2 . (Hint: you can use the fact that the same sinusoidal current flows through all resistors in a series circuit.)

[7 marks]

- (b) Figure 4.1 shows a Wheatstone bridge circuit. If all the resistors are equal to R , the bridge should be balanced and the output voltage (V_{OUT}) should be zero. State the relationship between the resistors, and then find R_2 if the bridge is balanced, and where $R_1 = 470 \Omega$, $R_3 = 330 \Omega$ and $R_4 = 270 \Omega$.

[4 marks]

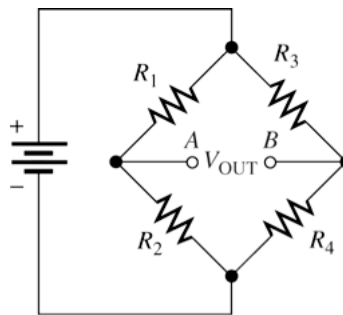


Figure 4.1

- (c) For the circuit shown in Figure 4.2, calculate:

(i) The total equivalent resistance R_T ,

[5 marks]

(ii) The current I_S ,

[2 marks]

(iii) The power dissipated across the resistor R_1 .

[2 marks]

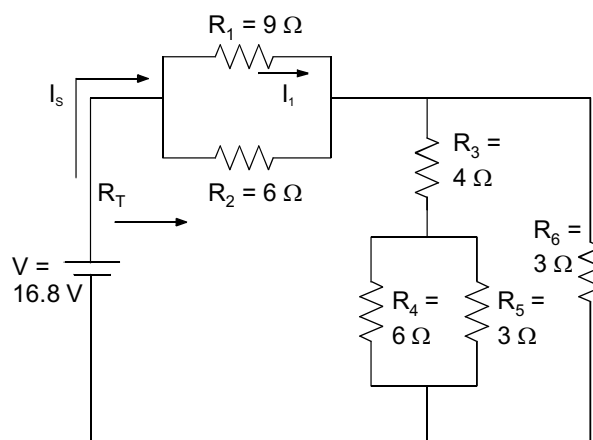


Figure 4.2

[20 marks in total]