



OLLSCOIL NA GAILLIMHÉ
UNIVERSITY OF GALWAY

CT101 Computing Systems

Dr. Bharathi Raja Chakravarthi

Lecturer-above-the-bar

Email: bharathi.raja@universityofgalway.ie



University
ofGalway.ie




OLLSCOIL NA GAILLIMHE
UNIVERSITY OF GALWAY

Other Two-Level Implementations

Introduction

 - In integrated circuits, NAND and NOR gates are commonly used.
- These gates often **allow wire connections between their outputs** to create specific logic functions, known as "**wired logic**."
- For example, open-collector TTL NAND gates perform wired-AND logic when connected together.
- The wired-AND logic performed with two NAND gates is depicted in Figure (a).




(a) Wired-AND in open-collector
TTL NAND gates.

(AND-OR-INVERT)



Introduction

- The **wired-AND logic is symbolically represented**, with lines passing through the center of the gate to distinguish it.
- The wired-AND gate is a symbolic representation of the function achieved through a specific wired connection, not a physical gate.
- The logic function implemented by this wired-AND gate is
$$\mathbf{F = (AB)'(CD) = (AB + CD) = (A + B)(C + D)}$$
- This function is referred to as an **AND-OR-INVERT function**.

 

(a) Wired-AND in open-collector
TTL NAND gates.


(AND-OR-INVERT)



Introduction

- ECL gates with NOR outputs can be connected to perform a **wired-OR function**.
- The logic function implemented by the circuit of Figure (b) is and is called an **OR-AND-INVERT** function.
 
$$F = (A + B)' + (C + D)' = [(A + B)(C + D)]'$$



(b) Wired-OR in ECL gates

(OR-AND-INVERT)



Introduction

- A wired-logic gate does **not produce a physical second-level gate**, since it is just a wire connection.
- For discussion purposes, we will consider the circuits of **Figure (a) and (b) as two-level implementations**.
- The **first level** consists of **NAND** (or **NOR**) gates and the **second level** has a single **AND** (or **OR**) gate.
- The wired connection in the graphic symbol will be omitted in subsequent discussions.



Nondegenerate Forms

- **Four types** of gates are considered: AND, OR, NAND, and NOR.
- When **one type** of gate is assigned for the **first level** and **one for the second level**, there are **16 possible combinations** of two-level forms.

Note:

The same type of gate can be in the first and second levels, as in a NAND–NAND implementation.

- **Eight of these combinations** are said to be **degenerate** forms because they degenerate to a single operation.



Nondegenerate Forms

- This can be seen from a circuit with AND gates in the first level and an AND gate in the second level.
- The output of the circuit is merely the AND function of all input variables.
- The remaining eight nondegenerate forms produce an implementation in sum-of-products form or product-of-sums form.



Nondegenerate Forms

- The **eight nondegenerate** forms are as follows:


| | |
|-----------|----------|
| AND-OR | OR-AND |
| NAND-NAND | NOR-NOR |
| NOR-OR | NAND-AND |
| OR-NAND | AND-NOR |

- The first gate listed in each of the forms **constitutes the first level in the implementation.**
- The second gate listed is a **single gate placed on the second level.**
- Note that any **two forms listed on the same line are duals of each other.**




AND-OR-INVERT Implementation

 
- **NAND-AND** and **AND-NOR** forms are equivalent and perform the **AND-OR-INVERT** function.
- The **AND-NOR** form resembles the **AND-OR** form but includes an inversion done by the bubble in the output of the NOR gate.
- It implements the function **$F = (AB + CD + E)'$** .



(a) AND-NOR

 

(b) AND-NOR

 


 (c) NAND-AND



AND-OR-INVERT Implementation

- The **alternative graphic symbol for the NOR gate** is used in the diagram (Figure b).
- A single variable, E , is not complemented in this diagram because the **only change is in the graphic symbol of the NOR gate**.
- The bubble from the input terminal of the second-level gate is moved to the output terminals of the first-level gates.




 (b) AND-NOR



AND-OR-INVERT Implementation

- An **inverter is needed for the single variable** to compensate for the bubble, or the inverter can be removed if input E is complemented.
- The circuit in Figure c is a **NAND-AND form**, which was previously shown to implement the AND-OR-INVERT function.




AND–OR–INVERT Implementation

- An AND–OR implementation requires an **expression in sum-of-products form**.
- The AND–OR–INVERT implementation is **similar to AND–OR, except for the inversion**.
- If the complement of the function is simplified into sum-of-products form (by combining the 0's in the map), **it will be possible to implement F' with the AND–OR part** of the function.
- When F' passes through the always present output inversion (the INVERT part), it will generate the output F of the function.
- An example for the AND–OR–INVERT implementation will be shown subsequently.




OR-AND-INVERT Implementation

 
- The **OR-NAND** and **NOR-OR** forms perform the **OR-AND-INVERT** function, as shown in Figure below.
- The **OR-NAND** form resembles the **OR-AND** form, except for the inversion done by the bubble in the NAND gate.
- It implements the function **$F = [(A + B)(C + D)E]'$**



(a) OR-NAND

 

(b) OR-NAND

 


 (c) NOR-OR



OR-AND-INVERT Implementation

- By using the **alternative graphic symbol for the NAND gate**, we obtain the diagram of Figure (b).
- The circuit in Figure (c) is **obtained by moving the small circles** from the inputs of the second-level gate to the outputs of the first-level gates.
- The circuit of Figure (c) is a NOR-OR form.



OR-AND-INVERT Implementation

- The OR-AND-INVERT implementation **requires an expression in product-of-sums** form.
- If the complement of the function is simplified into that form, we can implement F' with the OR-AND part of the function.
- When F' **passes through the INVERT** part, we obtain the complement of F' , or F , in the output.



Tabular Summary

- The Table below summarizes the procedures for implementing a Boolean function in any one of the four 2-level forms.
- Because of the INVERT part in each case, it is convenient to use the simplification of F' (the complement) of the function.

| Equivalent Nondegenerate Form | | Implements the Function | Simplify F' into | To Get an Output of |
|----------------------------------|----------|-------------------------------|---|---------------------------|
| (a) | (b)* | | | |
| AND-NOR | NAND-AND | AND-OR-INVERT | Sum-of-products form by combining 0's in the map. | F |
| OR-NAND | NOR-OR | OR-AND-INVERT | Product-of-sums form by combining 1's in the map and then complementing. | F |

*Form (b) requires an inverter for a single literal term.



Tabular Summary

- When F' is implemented in one of these forms, we obtain the complement of the function in the **AND-OR or OR-AND** form.
- The four 2-level forms invert this function, giving an output that is the complement of F .
- This is the normal output F .

| Equivalent Nondegenerate Form | | Implements the Function | Simplify F' into | To Get an Output of |
|----------------------------------|----------|-------------------------------|---|---------------------------|
| (a) | (b)* | | | |
| AND-NOR | NAND-AND | AND-OR-INVERT | Sum-of-products form by combining 0's in the map. | F |
| OR-NAND | NOR-OR | OR-AND-INVERT | Product-of-sums form by combining 1's in the map and then complementing. | F |

*Form (b) requires an inverter for a single literal term.



Example

Implement the function of $F = x'y'z' + xyz'$ with the four 2-level forms.

- The complement of the function is simplified into sum-of-products form by combining the 0's in the map:

$$F' = x'y + xy' + z$$


- The normal output for this function can be expressed as

$$F = (xy + xy' + z)$$



 Example

- The normal output is in the AND–OR–INVERT form. The AND–NOR and NAND–AND implementations are shown in Figure (b).
- Note that a **one-input NAND, or inverter, gate is needed in the NAND–AND** implementation, but **not in the AND–NOR case**.
- The **inverter can be removed** if we **apply the input variable z' instead of z** .




Example

- The OR–AND–INVERT forms **require a simplified expression** of the complement of the function in product-of-sum form.
- To obtain this expression, we **first combine the 1's in the map**:

$$F = x'y'z' + xyz'$$

 - Then we take the complement of the function: **$F' = (x + y + z)(x' + y' + z)$**




(b) $F = (x'y + xy' + z)'$



 Example

- The **normal output F** can now be expressed in the form **$F = [(x+y+z)(x' + y' + z)]$** which is the OR-AND-INVERT form.
- From this expression, **we can implement the function in the OR-NAND and NOR-OR forms**, as shown in Figure (c).



(c) $F = [(x + y + z)(x' + y' + z)]'$





OLLSCOIL NA GAILLIMHE
UNIVERSITY OF GALWAY

Exclusive-OR Function

Introduction

- The exclusive-OR (XOR), **denoted by the symbol \oplus** , is a logical operation that performs the following Boolean operation:

$$x \oplus y = xy' + x'y$$

- The **exclusive-OR is equal to 1 if only x is equal to 1 or if only y is equal to 1** (i.e., x and y differ in value), but **not when both are equal to 1 or when both are equal to 0**.
- The **exclusive NOR, also known as equivalence**, performs the following Boolean operation:

$$(x \oplus y)' = xy + x'y'$$



Introduction

- The exclusive-NOR is equal to 1 if both x and y are equal to 1 or if both are equal to 0.
- The exclusive-NOR can be shown to be the complement of the exclusive-OR by means of a truth table or by algebraic manipulation:

$$(x \oplus y)' = (xy' + x'y)' = (x' + y)(x + y') = xy + x'y'$$

- The following identities apply to the exclusive-OR operation:

$$x \oplus 0 = x$$

$$x \oplus 1 = x'$$

$$x \oplus x = 0$$

$$x \oplus x' = 1$$

$$x \oplus y' = x' \oplus y = (x \oplus y)'$$



Introduction

- Any of these identities can be proven with a truth table or by replacing the \oplus operation by its equivalent Boolean expression.
- It can be shown that the exclusive-OR operation is both commutative and associative; that is,

$$A \oplus B = B \oplus A \text{ and } (A \oplus B) \oplus C = A \oplus (B \oplus C) = A \oplus B \oplus C$$




Introduction

- In an exclusive-OR (XOR) gate, the **two inputs can be interchanged without affecting the operation.**
- A three-variable XOR operation can be evaluated in any order, **allowing the expression of three or more variables without parentheses.**
- This implies the possibility of **using exclusive-OR gates with three or more inputs.**
- However, **multiple-input exclusive-OR gates** are difficult to fabricate with hardware.
- Even a two-input function is typically **constructed with other types of gates.**




Introduction

 - A **two-input exclusive-OR function** is constructed with conventional gates using two inverters, two AND gates, and an OR gate, as shown in Figure (a).



(a) Exclusive-OR with AND-OR-NOT gates

 

(b) Exclusive-OR with NAND gates

- Figure (b) shows the implementation of the exclusive-OR with four NAND gates.
- The first NAND gate performs the operation **$(xy)' = (x' + y')$** .
- The other two-level NAND circuit produces the sum of products of its inputs:

$$(x' + y')x + (x' + y')y = xy' + x'y = x \oplus y$$



Introduction

- Only a **limited number** of Boolean functions can be expressed in terms of exclusive-OR (XOR) operations.
- The **XOR function** is encountered frequently in the design of digital systems.
- It is particularly **useful in arithmetic operations and error detection and correction** circuits.



Odd Function

- The exclusive-OR operation with three or more variables can be converted into an ordinary Boolean function by replacing the \oplus symbol with its equivalent Boolean expression.
- In particular, the three-variable case can be converted to a Boolean expression as follows:

$$\begin{aligned} A \oplus B \oplus C &= (AB' + A'B)C' + (AB + A'B')C \\ &= AB'C' + A'BC' + ABC + A'B'C \\ &= \Sigma(1, 2, 4, 7) \end{aligned}$$



Odd Function

- Three-variable exclusive-OR (XOR) function evaluates to 1 under two conditions:
 - When only one variable is equal to 1.
 - When all three variables are equal to 1.
- Unlike the two-variable XOR, where only one variable must be 1, in the case of three or more variables, an odd number of variables (1, 3, 5, etc.) must be equal to 1 for the function to yield 1.
- The multiple-variable exclusive-OR operation is defined as an "**odd function**."



Odd Function

- The three-variable exclusive-OR function is expressed as the logical sum of four minterms.
- These minterms have binary numerical values of **001, 010, 100, and 111**.
- All of these binary values have an odd number of 1's (1, 1, 1, and 3, respectively).
- The remaining four minterms (**000, 011, 101, and 110**) are not included in the function.
- These excluded minterms have an even number of 1's in their binary numerical values.
- In general, for an n-variable exclusive-OR function is an odd function defined as the logical sum of **$2^{n/2}$ minterms** whose binary numerical values have an odd number of 1's.



Odd Function

- The concept of an odd function can be clarified through mapping.
- Figure (a) illustrates the [map for the three-variable exclusive-OR](#) function.
- The four minterms of this function are equally spaced on the map.

| $A \backslash BC$ | | B | | | |
|-------------------|---|------------|------------|------------|------------|
| | | 00 | 01 | 11 | 10 |
| A | 0 | m_0 | m_1 1 | m_3 | m_2 1 |
| | 1 | m_4 1 | m_5 | m_7 1 | m_6 |

(a) Odd function $F = A \oplus B \oplus C$



Odd Function

- Odd functions are identified by the binary values of their minterms having an odd number of 1's.
- The complement of an odd function results in an even function.
- Figure (b) depicts a three-variable even function, which evaluates to 1 when an even number of its variables are set to 1, including the case where none of the variables is 1.


| | | BC | | | |
|-----|---|------------|------------|------------|------------|
| | | 00 | 01 | 11 | 10 |
| A | 0 | m_0 1 | m_1 | m_3 1 | m_2 |
| | 1 | m_4 | m_5 1 | m_7 | m_6 1 |

 (b) Even function $F = (A \oplus B \oplus C)'$




Odd Function

- A **three-input odd** function is implemented using **two-input exclusive-OR** gates (Figure (a)).
- The complement of an odd function is achieved by replacing the output gate with an exclusive-NOR gate (Figure (b)).
- Now, let's consider the four-variable exclusive-OR operation.



(a) 3-input odd function

 

(b) 3-input even function



Odd Function

- we can obtain the **sum of minterms** for this function:

$$\begin{aligned} A \oplus B \oplus C \oplus D &= (AB' + A'B) \oplus (CD' + C'D) \\ &= (AB' + A'B)(CD + C'D') + (AB + A'B')(CD' + C'D) \\ &= \Sigma(1, 2, 4, 7, 8, 11, 13, 14) \end{aligned}$$

- For a four-variable Boolean function, **there are 16 minterms**.
- Half of the minterms have binary numerical values with an **odd number of 1's**, and the **other half have an even number of 1's**.



Odd Function

- The binary value of a minterm is determined by its position in the map, based on row and column numbers.
- The map in Figure (a) represents the four-variable exclusive-OR function, which is an odd function.
- The complement of an odd function is an even function, as shown in Figure (b).

| AB \ CD | | C | | | |
|---------|----|------------|---------------|---------------|---------------|
| | | 00 | 01 | 11 | 10 |
| A | 00 | m_0 | m_1 1 | m_3 | m_2 1 |
| | 01 | m_4 1 | m_5 | m_7 1 | m_6 |
| | 11 | m_{12} | m_{13} 1 | m_{15} | m_{14} 1 |
| | 10 | m_8 1 | m_9 | m_{11} 1 | m_{10} |
| | | D | | | |

(a) Odd function $F = A \oplus B \oplus C \oplus D$

| AB \ CD | | C | | | |
|---------|----|---------------|------------|---------------|---------------|
| | | 00 | 01 | 11 | 10 |
| A | 00 | m_0 1 | m_1 | m_3 1 | m_2 |
| | 01 | m_4 | m_5 1 | m_7 | m_6 1 |
| | 11 | m_{12} 1 | m_{13} | m_{15} 1 | m_{14} |
| | 10 | m_8 | m_9 1 | m_{11} | m_{10} 1 |
| | | D | | | |

(b) Even function $F = (A \oplus B \oplus C \oplus D)'$



Parity Generation and Checking

- Exclusive-OR (XOR) functions have practical applications in systems requiring error detection and correction codes.
- A parity bit is commonly used for error detection during the transmission of binary information.
- A parity bit is an additional bit added to a binary message to ensure that the total number of 1's in the message (including the parity bit) is either odd or even.



Parity Generation and Checking

- The transmitted message, along with the parity bit, is **received and checked for errors** at the receiving end.
- Error detection occurs when the checked parity **doesn't match the transmitted one**.
- The **circuit responsible for generating the parity bit in the transmitter is called a "parity generator."**
- The **circuit in the receiver that verifies the parity is known as a "parity checker."**



Parity Generation and Checking

- An example involves a three-bit message transmitted with an even-parity bit.
- The truth table for the parity generator is shown in the Table below.
- The three bits, labeled as x , y , and z , form the message and serve as inputs to the circuit.
- The output is the parity bit P .

Even-Parity-Generator Truth Table

| Three-Bit Message | | | Parity Bit |
|-------------------|-----|-----|------------|
| x | y | z | P |
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 |



Parity Generation and Checking

- For even parity, P is generated to ensure the total number of 1's (including P) is even.
- P is determined by minterms with an odd number of 1's in their binary values.
- This makes P an odd function, as it equals 1 for minterms with an odd number of 1's.
- Therefore, P can be expressed as a three-variable exclusive-OR function:

$$P = x \oplus y \oplus z$$


Even-Parity-Generator Truth Table

| Three-Bit Message | | | Parity Bit |
|-------------------|----------|----------|------------|
| <i>x</i> | <i>y</i> | <i>z</i> | <i>P</i> |
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 |



Parity Generation and Checking

 - The logic diagram for the parity generator is shown in Fig. (a)



(a) 3-bit even parity generator

- Data transmission involves sending three data bits along with a parity bit for error checking.
- At the destination, a parity-checker circuit is used to examine the received bits for potential errors.



Parity Generation and Checking

- In this case, even parity is utilized, meaning that the **four bits received must contain an even number of 1's**.
- An error during transmission is identified if the four received bits contain an odd number of 1's, suggesting that a bit has changed value during the transmission.
- The **output of the parity checker is denoted as "C," and it equals 1** if an error occurs, indicating that the four received bits have an odd number of 1's.



Parity Generation and Checking

- The table presents the truth table for the even-parity checker, outlining the conditions under which C is equal to 1.

| Four Bits Received | | | | Parity Error Check |
|--------------------|----------|----------|----------|--------------------|
| <i>x</i> | <i>y</i> | <i>z</i> | <i>P</i> | <i>C</i> |
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 1 | 1 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 0 |
| 1 | 0 | 1 | 1 | 1 |
| 1 | 1 | 0 | 0 | 0 |
| 1 | 1 | 0 | 1 | 1 |
| 1 | 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 | 0 |



Parity Generation and Checking

- The function C is defined by the eight minterms with binary numerical values that have an odd number of 1's.
- This truth table corresponds to the map shown in Fig. (a), which represents an odd function.

| $AB \backslash CD$ | | C | | | |
|--------------------|----|------------|---------------|---------------|---------------|
| | | 00 | 01 | 11 | 10 |
| A | 00 | m_0 | m_1 1 | m_3 | m_2 1 |
| | 01 | m_4 1 | m_5 | m_7 1 | m_6 |
| | 11 | m_{12} | m_{13} 1 | m_{15} | m_{14} 1 |
| | 10 | m_8 1 | m_9 | m_{11} 1 | m_{10} |
| | | D | | | |

(a) Odd function $F = A \oplus B \oplus C \oplus D$




Parity Generation and Checking

- The parity checker can be implemented with exclusive OR gates:

$$C = x \oplus y \oplus z \oplus P$$

 - The logic diagram of the parity checker is shown in Fig. (b).




 (b) 4-bit even parity checker



Parity Generation and Checking

- The parity generator can be efficiently implemented using the circuit depicted in Fig. (b) when the input P is set to logic 0, and the output is designated as P .
- This implementation is feasible because $z \oplus 0 = z$, meaning that the value of z passes through the gate without alteration.
- An important advantage of this approach is its versatility, as the same circuit can serve the dual purpose of both parity generation and checking.



(b) 4-bit even parity checker



References

- Computer Organization and Architecture Designing for Performance Tenth Edition by William Stallings
- Digital Design With an Introduction to the Verilog HDL FIFTH EDITION by M Morris, M. and Michael, D., 2013.





OLLSCOIL NA GAILLIMHÉ
UNIVERSITY OF GALWAY

Thank *you*