



OLLSCOIL NA GAILLIMHÉ
UNIVERSITY OF GALWAY

CT101 Computing Systems

Dr. Bharathi Raja Chakravarthi

Lecturer-above-the-bar

Email: bharathi.raja@universityofgalway.ie



University
ofGalway.ie



OLLSCOIL NA GAILLIMHE
UNIVERSITY OF GALWAY

Binary Adder-Subtractor

Introduction

Basic Arithmetic in Digital Computers:

- Computers perform various arithmetic operations; the most fundamental is binary addition.

Binary Addition Operations:

- **Four basic calculations:**
 - $0 + 0 = 0$
 - $0 + 1 = 1$
 - $1 + 0 = 1$
 - $1 + 1 = 10$ (produces a 'carry' bit)



Introduction

Carry Bit:

- In binary addition, when both digits are 1, the result is a two-digit number (10), with the '1' becoming the carry bit for the next significant digit pair.

Half Adder:

- A combinational circuit that **adds two single binary digits**.
- Does not account for carries from previous digits.



Introduction

Full Adder:

- Handles the addition of three bits: two significant bits and one carry bit from the addition of the previous lower significant bits.
- Two half adders can be combined to create a full adder.



Introduction

- A **binary adder–subtractor** is a combinational circuit that performs the arithmetic operations of addition and subtraction with binary numbers.
- We will develop this circuit by means of a hierarchical design.
- The **half adder design is carried out first**, from which we **develop the full adder**.



Introduction

Creating an Adder for n-bit Numbers:

- n full adders are connected in a cascade configuration to add two n-bit binary numbers.

Subtraction Capability:

- Subtraction is facilitated by incorporating a complementing circuit that works with the adders.
- This design uses the concept of two's complement for binary subtraction.



Half Adder

- A digital circuit with two binary inputs and two binary outputs.
- Inputs represent two single binary digits (bits) to be added.
- Outputs produce the resulting sum and the carry bit.

Input/Output Designation:

- Inputs: x and y
- Outputs: S (sum) and C (carry)



Half Adder

Truth Table:

- Details the logic of the half-adder operation.
- Output C is high (1) only when both x and y are high (1).
- Output S represents the binary sum without the carry.

x	y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0





Half Adder

Boolean Functions:

- Sum **(S)**= $x'y + xy'$ (using XOR logic)
- Carry **(C)**= xy (using AND logic)

Logic Diagrams:

  - Two representations:
 - Sum of products with AND, OR, and NOT gates (Fig. (a)).
 - With an exclusive-OR (XOR) for the sum and an AND gate for the carry (Fig. (b)).
- Illustrates how two half-adders can be integrated to form a full adder.



Full Adder

- A digital circuit that **computes the arithmetic sum of three input bits**.
- Used for bit-by-bit addition of n -bit binary numbers, considering carry.

Input/Output Designation:

- **Inputs:** x , y (significant bits), z (carry from previous addition)
- **Outputs:** S (sum), C (carry)



Full Adder

Functionality:

- Adds bits x , y , and z to produce a two-bit result (as binary sums can range from 0 to 3).
- Output S is the least significant bit of the sum.
- Output C represents the carry-out of the addition.

Truth Table:

- Eight rows representing all possible combinations of three inputs
- Outputs are derived based on the binary sum of input bits.

x	y	z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1



Full Adder

Outputs Interpretation:

- In terms of **binary addition and Boolean function** variables.
- Outputs S and C have different interpretations **depending on context** (binary addition vs. Boolean logic).

Boolean Expressions:


- Sum (S): **$S = x'y'z + x'yz' + xy'z' + xyz$**
- Carry (C): **$C = xy + xz + yz$**




Full Adder

- **Implementation Diagrams:**

 - Sum-of-products with logic gates (Fig. 4.7).



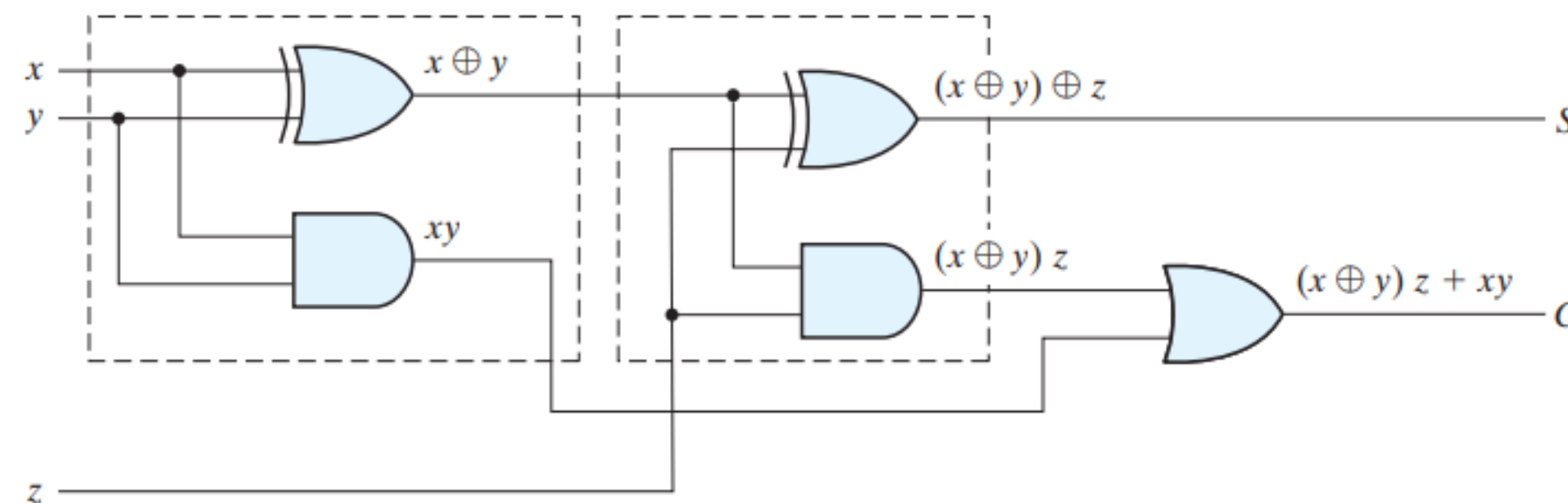- Using two half adders and an OR gate (Fig. 4.8).



Full Adder

Exclusive-OR for Output S :

- S is the XOR of z and the sum output of the first half adder.
- Expressed as $S = z \oplus (x \oplus y)$

$$\begin{aligned} &= z'(xy' + x'y) + z(xy' + x'y)' \\ &= z'(xy' + x'y) + z(xy + x'y') \\ &= xy'z' + x'yz' + xyz + x'y'z \end{aligned}$$

Carry Output (C):

- C is the OR of the carry outputs from both half adders and the AND of x and y .
- Simplified to $C = z(xy' + x'y) + xy$
 $= xy'z + x'yz + xy$




Binary Adder

- A digital circuit is designed to **compute the sum of two binary numbers**.
- Built by connecting full adders in series, with each full adder's carry-out connected to the next full adder's carry-in.

Construction:

 - Requires **n full adders to add two n -bit** numbers.
- For a 4-bit adder, **four full adders are interconnected** as shown in Figure below.
- The **least significant full adder receives an input carry** (denoted C_0), typically set to 0.



Binary Adder

Operation:

- Augend (A) and addend (B) bits are labeled from right to left, with the least significant bit as subscript 0.
- Carries ripple from one full adder to the next in sequence, from C_0 to C_4 .

Example Calculation with A = 1011 and B = 0011:

- Start with the least significant bit: $A_0 = 1$, $B_0 = 1$ plus the initial carry $C_0 = 0$.
- The first full adder computes S_0 and generates a carry C_1 for the next position.
- This process continues for each bit, with carries rippling to the next full adder.
- The final sum bits (S) are generated in sequence, resulting in $S = 1110$.



Subscript i:	3	2	1	0	
Input carry	0	1	1	0	C_i
Augend	1	0	1	1	A_i
Addend	0	0	1	1	B_i
Sum	1	1	1	0	S_i
Output carry	0	0	1	1	C_{i+1}

Binary Adder

Carry Operation:

- **Initial Carry:** The carry-in for the **LSB (C_0)** is set to 0.
- **Sequential Carry:** The carry-out from each full adder (C_i) becomes the carry-in for the next significant bit's full adder (C_{i+1}).
- **Propagation:** Carry values ripple through from right to left, which is why it's called a ripple carry adder.

Sum Generation:

- The sum bits (S) are produced in sequence from the **rightmost to the leftmost position**.
- The correctness of each sum bit relies on the carry generated from the addition of the previous bits.



Binary Adder

Efficiency:

- **Iterative Design:** Using a standard full adder repeatedly **avoids the complexity of designing** a new circuit for each application.
- **Simplifies Implementation:** Cascading standard full adders significantly **reduces design complexity compared** to creating a truth table for all input combinations, which would be **impractical for large bit sizes** (e.g., a truth table with 512 entries for a 4-bit adder).


Applications:

- The 4-bit adder can be employed in various arithmetic operations and is a **staple in digital system design**.
- Its standard component nature makes it a **building block in more complex arithmetic circuits**.




Carry Propagation

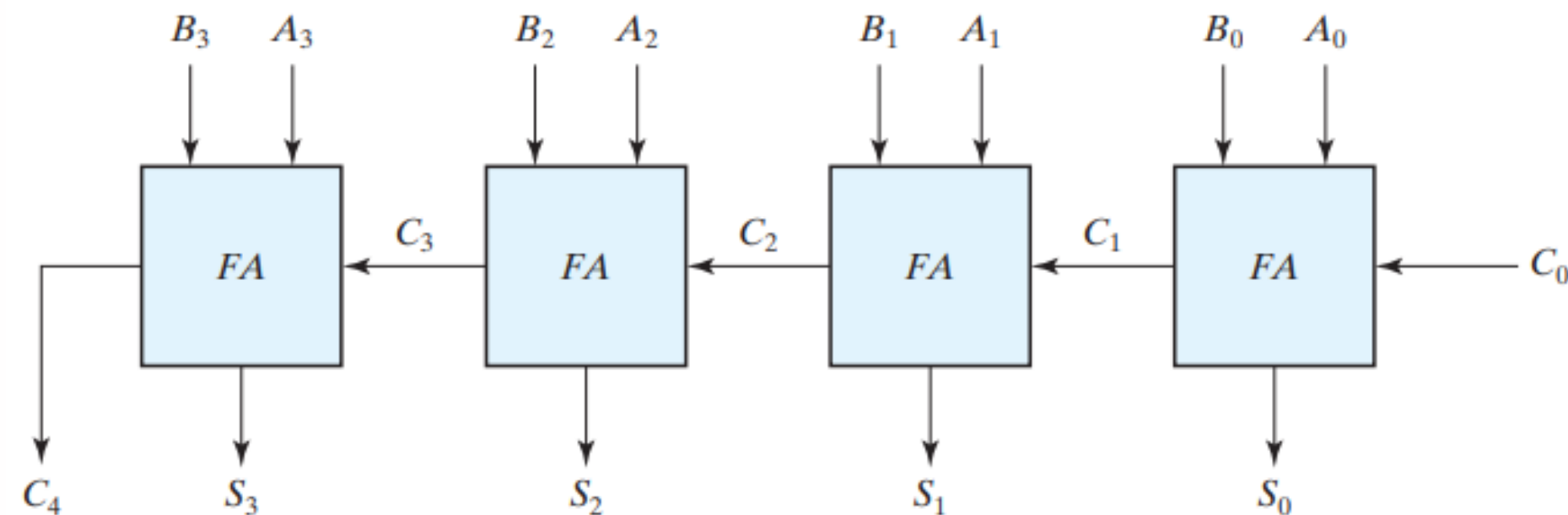- **Parallel Binary Addition:** All bits (augend and addend) are processed simultaneously (see Fig below).
- **Signal Propagation:** Correct sums after signals pass through gates (total time = gate delay \times number of gate levels).
- **Carry Propagation Delay:** Longest delay from carry bit passing through all full adders.




Carry Propagation

- **Output Sum Dependence:** Sum bit S_i final only after carry input C_i is stable.
- **Carry Ripple Effect:**
 - Output S_3 accuracy dependent on carry C_3 , which awaits C_2 from previous stage (see Fig. below).
 - This dependency chain continues back to carry C_0 .
- **Final Output:** S_3 and carry C_4 accurate after full carry ripple (carry propagation through 2_n gate levels for an n -bit adder).

 

Carry Propagation

- Circuit in Figure below shows carry signal progression through gate levels.
- Each stage, labeled with subscript i , adds two gate levels (AND and OR gates) for carry progression.
- P_i and G_i signals stabilize after passing through their respective gates.
- In a 4-bit adder, C_4 results after 8 gate levels (2 gate levels per adder stage).
- General formula: For an n -bit adder, carry signal propagates through 2_n gate levels from C_0 to C_n .

 

Carry Propagation

Speed Limitations Due to Carry Propagation:

- Carry propagation time is crucial for adder speed—**directly impacts how fast two numbers can be added.**
- Correct outputs **require enough time for signal** propagation through the gates (from inputs to outputs).
- This is vital since all arithmetic operations build on addition; thus, addition speed is a bottleneck.



Carry Propagation


- **Solutions to reduce delay include:**
 - Using faster gates with lower delay times (though there's a physical limit to gate speed).
 - Increasing circuit complexity to decrease carry delay time.
- The carry lookahead logic is a prevalent method for minimizing carry delay in parallel adders.



Carry Propagation

- Consider the circuit of the full adder shown in Figure below. If we define two new binary variables
 
$$P_i = A_i \oplus B_i$$
$$G_i = A_i B_i$$



Carry Propagation

- The output sum and carry can respectively be expressed as

$$\begin{aligned} S_i &= P_i \oplus C_i \\ C_{i+1} &= G_i + P_i C_i \end{aligned}$$

- G_i (carry generate) produces a carry of 1 when both A_i and B_i are 1, regardless of the input carry C_i .
- P_i (carry propagate) determines whether a carry into stage i will propagate into stage $i + 1$ (i.e., whether an assertion of C_i will propagate to an assertion of C_{i+1}).



Carry Propagation

- We now write the Boolean functions for the carry outputs of each stage and substitute the value of each C_i from the previous equations:

$$C_0 = \text{input carry}$$

$$C_1 = G_0 + P_0 C_0$$

$$C_2 = G_1 + P_1 C_1 = G_1 + P_1 (G_0 + P_0 C_0) = G_1 + P_1 G_0 + P_1 P_0 C_0$$


$$C_3 = G_2 + P_2 C_2 = G_2 + P_2 G_1 + P_2 P_1 G_0 = P_2 P_1 P_0 C_0$$

- The Boolean function for each output carry is represented in sum-of-products form.
- Each function can be implemented with one level of AND gates followed by an OR gate, or alternatively, a two-level NAND gate.




Carry Propagation

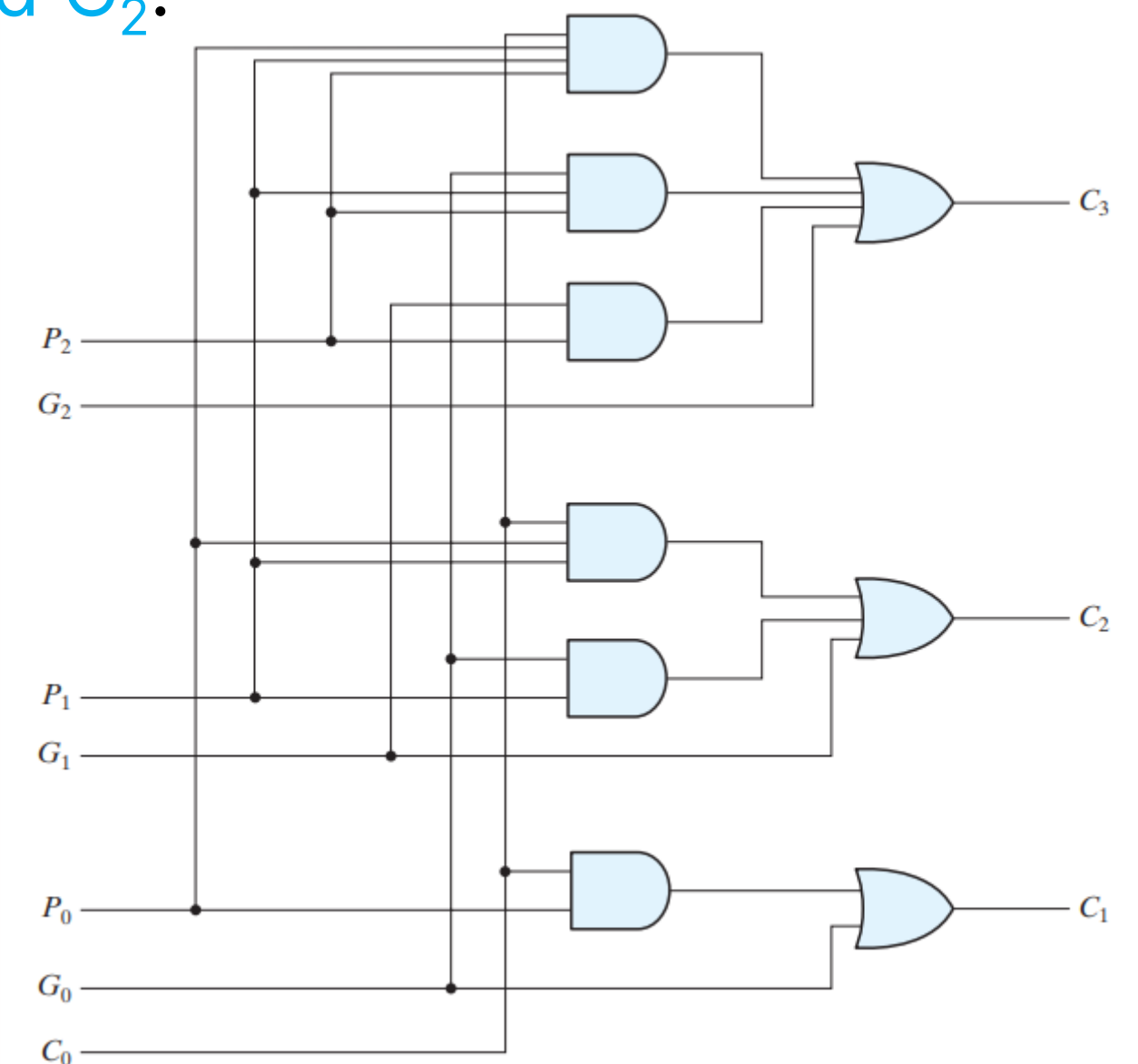- The carry lookahead generator, depicted in Fig. 4.11, is used to implement the three Boolean functions for C_1 , C_2 , and C_3 .
- Notably, this circuit speeds up addition as C_3 no longer needs to wait for C_2 and C_1 to propagate. Instead, C_3 is propagated simultaneously with C_1 and C_2 .
- This improved speed comes at the cost of increased complexity in hardware.



Carry Propagation

 - The construction of a **four-bit adder with a carry-lookahead** scheme is depicted in Figure.
- For each sum output, **two exclusive-OR gates are used**.
- The **first exclusive-OR gate generates the P_i variable**, while the AND gate produces the G_i variable.
- **Carries are propagated through a carry-lookahead generator**, similar to the one shown in Figure in the previous slide.



Carry Propagation

- These **generated carries serve as inputs** to the second exclusive-OR gate.
- **All output carries experience a delay through two levels** of gates, resulting in equal propagation delay times for outputs S1 through S3.
- While not shown, the two-level circuit for output carry C4 can be **derived using the equation-substitution method**.



Binary Subtractor

- Subtraction of two numbers, $A - B$, is performed by adding A to the 2's complement of B .

Finding the 2's Complement:

- Obtain the 1's complement of B by inverting all bits.
- Add 1 to the least significant bit (LSB) of the inverted B to get the 2's complement.



Binary Subtractor

Circuit Implementation:

- An adder circuit is used, where each bit of B is inverted before entering the adder.
- The input carry C_0 is set to 1 to account for the +1 needed in the 2's complement process.

Subtraction Operation:

- The circuit performs A plus the 1's complement of B plus 1, which results in A plus the 2's complement of B .



Binary Subtractor


Results Interpretation:

- For unsigned numbers: The result is $A-B$ if A is greater than or equal to B , or the 2's complement of $B-A$ if A is less than B .
- For signed numbers: The result is correct as $A-B$ provided there is no overflow in the operation.



Binary Subtractor

- **Common Circuit with Exclusive-OR Gate:**
 - Addition and subtraction can be integrated into one circuit using a binary adder with an **exclusive-OR gate** at each full adder.
- **Four-Bit Adder-Subtractor Circuit referenced in Figure**, the circuit operates based on a mode input M .
- **Mode Input M Functionality:**
 - If $M=0$: The circuit acts as an adder.
 - If $M=1$: The circuit functions as a subtractor.

 

Binary Subtractor

Exclusive-OR Gate Role:

- Each exclusive-OR gate takes in the **mode input M** and **one of the B inputs**.
- When **$M=0: B \oplus 0=B$** . The full adders get the B value with input carry as 0. The operation becomes **$A+B$** .
- When **$M=1: B \oplus 1=B'$** (complement of B) and **$C_0=1$** . All B inputs are inverted, and 1 is added via the input carry. This results in the operation A plus the 2's complement of B.



Binary Subtractor

- **Overflow Detection:**
An exclusive-OR gate with an output V is included to identify overflow situations.
- **Signed-Complement System and Binary Arithmetic:**
 - Binary numbers in the signed-complement system use the same basic rules for addition and subtraction as unsigned numbers.
 - Computers need only one unified hardware circuit to perform both types of arithmetic.
 - The interpretation of results varies based on the assumed number type (signed or unsigned).



Overflow

- **Definition of Overflow:**
 - Overflow happens when adding two numbers with n digits each results in a sum occupying $n+1$ digits.
 - This applies to both binary and decimal numbers, whether they're signed or unsigned.
- **Paper vs. Digital Overflow:**
 - While doing arithmetic manually (e.g., using paper and pencil), overflow isn't a concern because there's no fixed width constraint like in digital systems.
 - In contrast, digital computers have a fixed bit-width to store numbers, making overflow a significant issue.



Overflow

- **Overflow Detection in Computers:**

- Computers can detect overflow, typically **setting a specific flip-flop** (or flag) to signal it.
- Users or programs can then check this **flag to ascertain if an overflow has occurred** during computation.

- **Overflow in Unsigned vs. Signed Numbers:**

- **Unsigned Numbers:** Overflow is detected from the end carry-out of the most significant position.
- **Signed Numbers:**
 - The leftmost bit **represents the sign, and negative numbers are typically in 2's-complement form.**
 - The **end carry doesn't indicate an overflow for signed numbers** because the leftmost bit is part of the number itself.



Overflow

Overflow Scenarios with Signed Numbers:

- **Different Signs:**
 - Overflow can't happen if one number is positive and the other is negative.
 - The result's magnitude will always be less than the magnitude of the larger original number.
- **Same Signs:**
 - Overflow can occur if both numbers being added are positive or both are negative.
 - For instance, adding two signed numbers, +70 and +80, stored in two eight-bit registers can lead to an overflow because the sum (+150) exceeds the register's capacity, which ranges from +127 to -128.



Overflow

The two additions in binary are shown next, together with the last two carries:

carries:	0 1
+70	0 1000110
+80	0 1010000
<hr/>	<hr/>
+150	1 0010110

carries:	1 0
−70	1 0111010
−80	1 0110000
<hr/>	<hr/>
−150	0 1101010

Note that

- the **eight-bit result that should have been positive has a negative sign bit** (i.e., the eighth bit) and the eight-bit result that should have been **negative** has a positive sign bit.
- If, however, the **carry out of the sign bit position is taken as the sign bit of the result**, then the nine-bit answer so obtained will be correct.
- But since the answer **cannot be accommodated within eight bits**, we say that an **overflow has occurred**.



Overflow


- The presence of overflow in binary addition of signed numbers can be **determined by comparing the carry into the sign bit position** with the carry out of the sign bit position.
- If they are different, it indicates an overflow condition. Conversely, if they are the same, no overflow occurred.
- **Exclusive-OR Gate for Detection:**
 - By using an exclusive-OR (XOR) gate on the **carry into and carry out of the sign bit**, **overflow can be easily detected**.
 - If the **XOR gate outputs a '1'**, it's a **clear indication of overflow**. But if it outputs a '0', **no overflow has taken place**.
 - This method is reliable only when **2's-complement notation is used for representing negative numbers**, ensuring proper calculation of negative number complements



Overflow

Binary Adder-Subtractor Circuit:

- The reference to Figure likely depicts a circuit diagram of a **binary adder-subtractor**, showcasing its key outputs: C (Carry) and V (Overflow).
- The 'C' bit is primarily **used for detecting carry (in addition) or borrow (in subtraction)** for unsigned numbers.
- The '**V**' bit is **dedicated to detecting overflow conditions** when dealing with signed numbers.
- If after a computation, $V = 0$, it means the result is valid without any overflow. However, if $V = 1$, it indicates an overflow condition.

 

Overflow

Result Implication:

- When $V = 1$ after an operation, it means that the resultant value needs $n+1$ bits for accurate representation.
- However, given that only n bits are available for storage, the extra bit (which in the case of signed numbers represents the actual sign) is effectively shifted out, causing an overflow.



References

- Computer Organization and Architecture Designing for Performance Tenth Edition by William Stallings
- Digital Design With an Introduction to the Verilog HDL FIFTH EDITION by M Morris, M. and Michael, D., 2013.





OLLSCOIL NA GAILLIMHÉ
UNIVERSITY OF GALWAY

Thank *you*