



OLLSCOIL NA GAILLIMHÉ
UNIVERSITY OF GALWAY

CT101 Computing Systems

Dr. Bharathi Raja Chakravarthi

Lecturer-above-the-bar

Email: bharathi.raja@universityofgalway.ie



University
ofGalway.ie



OLLSCOIL NA GAILLIMHE
UNIVERSITY OF GALWAY

NAND and NOR Implementation



Introduction

- Digital circuits are frequently constructed with NAND or NOR gates rather than with AND and OR gates.
- NAND and NOR gates are easier to fabricate with electronic components and are the basic gates used in all IC digital logic families.
- Rules and procedures have been developed for the conversion from Boolean functions given in terms of **AND, OR, and NOT** into equivalent **NAND and NOR** logic diagrams.



NAND Circuits

  - The **NAND gate** is said to be a **universal gate** because any logic circuit can be implemented with it.
- To show that **any Boolean function can be implemented with NAND gates**, we need only show that the logical operations of AND, OR, and complement can be obtained with NAND gates alone.
- This is indeed shown in Figure.




NAND Circuits


- The complement operation is **obtained from a one-input NAND** gate that behaves exactly like an inverter.



 - The AND operation requires two NAND gates.
- The **first produces the NAND operation and the second inverts** the logical sense of the signal.



 - The OR operation is achieved through a NAND gate with additional inverters in each input.





NAND Circuits

- A convenient way to implement a Boolean function with NAND gates is to obtain the simplified Boolean function in terms of Boolean operators and then convert the function to NAND logic.
- The conversion of an algebraic expression from AND, OR, and complement to NAND can be done by simple circuit manipulation techniques that change AND–OR diagrams to NAND diagrams.




NAND Circuits

  - To facilitate the conversion to NAND logic, defining an **alternative graphic symbol** for the **gate** is convenient.
- **Two equivalent graphic symbols** for the NAND gate are shown in Figure.




NAND Circuits

 

 (a) AND-invert

- The **AND-invert symbol** has been defined previously and consists of an AND graphic symbol followed by a small circle negation indicator referred to as a bubble.



(b) Invert-OR


- The **invert-OR symbol** for the NAND gate follows DeMorgan's theorem and the convention that the negation indicator (bubble) denotes complementation.
- The two graphic symbols' representations are useful in analyzing and designing NAND circuits.
- When both symbols are mixed in the same diagram, the circuit is said to be in mixed notation.




Two-Level Implementation

- The implementation of Boolean functions with NAND gates requires that the functions be in sum-of-products form.
- To see the relationship between a sum-of-products expression and its equivalent NAND implementation, consider the logic diagrams drawn in Figure below.
- All three diagrams are equivalent and implement the function


$$F = AB + CD$$

 

(a)

 

(b)

 


(c)




Two-Level Implementation

 - The function $F = AB + CD$ is implemented in Fig. (a) with AND and OR gates.





 - In Fig. (b), the AND gates are replaced by NAND gates and the OR gate is replaced by a NAND gate with an OR-invert graphic symbol.




Two-Level Implementation

  
- Remember that a **bubble denotes complementation** and **two bubbles along the same line represent double complementation**, so both can be removed.
- Removing the bubbles on the gates of (b) produces the circuit of (a).
- Therefore, the two diagrams implement the same function and are equivalent.



Two-Level Implementation

 

 
- In Figure (c), the output NAND gate is redrawn with the AND-invert graphic symbol.
- In drawing NAND logic diagrams, the circuit shown in either Figure (b) or (c) is acceptable.
- The one in Figure (b) is in mixed notation and represents a more direct relationship to the Boolean expression it implements.



Two-Level Implementation

- The NAND implementation in Figure (c) can be verified algebraically.
- The function it implements can easily be converted to the sum-of products form by DeMorgan's theorem:

$$F = ((AB)(CD)) = AB + CD$$

 

(c)




Example

Implement the following Boolean function with NAND gates:

$$F(x, y, z) = (1, 2, 3, 4, 5, 7)$$


- The first step is to **simplify the function into the sum-of-products** form.
- This is done by means of the map of Figure (a), from which the simplified function is obtained:

$$F = xy + xy + z$$

 

 
Example

- The two-level NAND implementation is shown in Figure (b) in mixed notation.
- Note that input z must have a one-input NAND gate (an inverter) to compensate for the bubble in the second-level gate.



 Example

- An **alternative way of drawing** the logic diagram is given in Figure (c).
- Here, **all the NAND gates** are drawn with the **same graphic symbol**.
- The **inverter with input z has been removed**, but the **input variable is complemented** and **denoted by z'** .



(c)



Example

The procedure for obtaining the logic diagram from a Boolean function is as follows:

1. Simplify the function and **express it in sum-of-products** form.
2. **Create a NAND gate for each product** term with at least two literals. Use the literals as inputs to these gates, forming the first level.
3. Draw a **single gate using the AND-invert or invert-OR graphic symbol for the second level**, with inputs connected from outputs of first-level gates.
4. If a term has a single literal, **add an inverter in the first level**. However, if the single literal is complemented, it **can be connected directly to an input of the second-level NAND gate**.



Multilevel NAND Circuits

- The **standard form** of expressing Boolean functions results in a **two-level implementation**.
- In some cases, the design of digital systems may **require gating structures with three or more logic levels**.
- The most common procedure in the **design of multilevel circuits** is to express the Boolean function in terms of AND, OR, and complement operations.



Multilevel NAND Circuits


- The function can then be implemented with AND and OR gates.
- After that, if necessary, it can be converted into an all-NAND circuit.
- Consider, for example, the Boolean function

$$F = A (CD + B) + BC'$$



Multilevel NAND Circuits

- Although it is possible to remove the parentheses and reduce the expression into a standard sum-of-products form, **we choose to implement it as a multilevel circuit for illustration.**
- The AND–OR implementation is shown in Figure below. There are **four levels of gating** in the circuit.
- The **first level has two AND** gates.
- The **second level has an OR gate** followed by an **AND gate** in the third level and an **OR gate** on the fourth level.

 


 (a) AND–OR gates



Multilevel NAND Circuits

- A logic diagram with a pattern of alternating levels of AND and OR gates **can easily be converted into a NAND** circuit with the **use of mixed notation**, shown in Figure below.




(b) NAND gates

- The procedure is to **change every AND gate to an AND-invert** graphic symbol and every **OR gate to an invert-OR** graphic symbol.



Multilevel NAND Circuits

 - The **NAND** circuit performs the same logic as the **AND-OR** diagram as long as there are **two bubbles** along the same line.
- The bubble associated with input B causes extra complementation, which must be compensated for by changing the input literal to B .




(b) NAND gates



Multilevel NAND Circuits

The general procedure for converting a multilevel **AND–OR** diagram into an **all-NAND** diagram using mixed notation is as follows:

 1. Convert all AND gates to NAND gates with AND-invert graphic symbols.
2. Convert all OR gates to NAND gates with invert-OR graphic symbols.
3. Check all the bubbles in the diagram. For every bubble that is not compensated by another small circle along the same line, do one of the following:
 - Insert an inverter (a one-input NAND gate).
 - Complement the input literal associated with the bubble.



(b) NAND gates




Multilevel NAND Circuits

Another example, consider the multilevel Boolean function


$$F = (AB + AB)(C + D)$$

 - The **AND–OR** implementation of above function is shown in Figure with three levels of gating.



 (a) AND–OR gates


- The **conversion to NAND with mixed notation** is presented in Figure of the diagram.



(b) NAND gates



Multilevel NAND Circuits

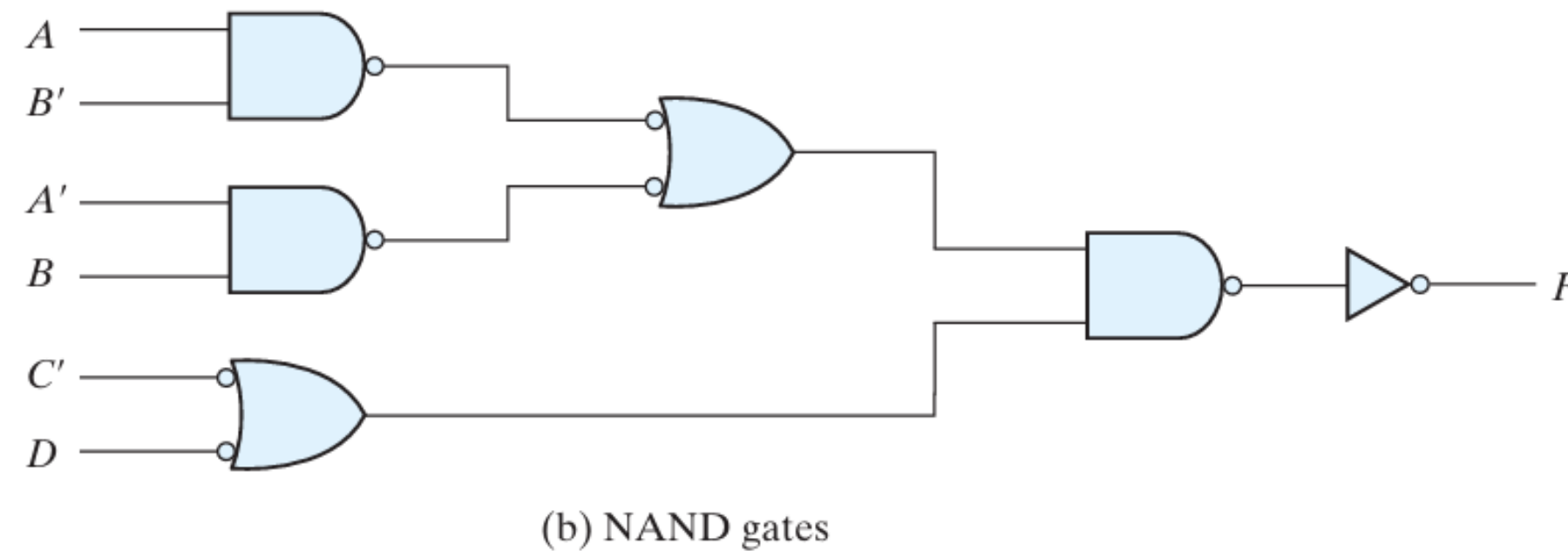

- The **two additional bubbles** associated with inputs C and D cause these two literals **to be complemented by C and D**.
- The bubble in the output NAND gate complements the output value, so we **need to insert an inverter gate at the output in order to complement the signal again** and get the original value back.





NOR Implementation

- The **NOR** operation is the **dual of the NAND** operation.
- Therefore, all procedures and **rules for NOR logic** are the **duals of the corresponding procedures and rules developed for NAND logic**.
- The NOR gate is another universal gate that can be used to implement any Boolean function.



NOR Implementation

  
- The **implementation of the complement, OR, and AND operations with NOR** gates is shown in Figure below.
- The complement operation is obtained from a **one input NOR gate that behaves exactly like an inverter**.
- The **OR operation requires two NOR gates**, and the **AND operation is obtained with a NOR gate that has inverters in each input**.



NOR Implementation


Two graphic symbols for the mixed notation:

 - The OR-invert symbol defines the **NOR operation as an OR followed by a complement**.



 (a) OR-invert

- The invert-AND symbol **complements each input and then performs an AND operation**.



(b) Invert-AND

- The two symbols designate the same NOR operation and are logically identical **because of DeMorgan's theorem**.



NOR Implementation

- To transform a two-level implementation with NOR gates, you need to first simplify the function into product-of-sums form.
- This simplified expression is derived from the map by combining the **0's** and applying complements as needed.
- Once you have the product-of-sums expression, you can implement it with a two-level structure consisting of OR gates and an AND gate.



NOR Implementation

- To convert this **OR-AND** diagram into a **NOR** diagram, follow these steps:
 1. Change all OR gates to NOR gates using the OR-invert graphic symbols.
 2. Change the AND gate to a NOR gate using the invert-AND graphic symbol.
- This transformation allows you to create a circuit using **NOR** gates while maintaining the logic of the original **product-of-sums** expression.
- It's a useful technique when working with NOR gate-based digital logic design.




NOR Implementation

- A **single literal term** going into the **second-level** gate must be complemented.
- The Below Figure shows the **NOR** implementation of a function expressed as a product of sums:

$$F = (A + B)(C + D)E$$

 - The OR–AND pattern can easily be detected by the removal of the bubbles along the same line.
- Variable **E** is complemented to compensate for the third bubble at the input of the second-level gate.



NOR Implementation



- The procedure of converting a multilevel AND-OR diagram to an all-NOR diagram is **analogous to the transformation for NAND** gates.
- To achieve this for NOR gates, follow these steps:
 1. Change each OR gate to an OR-invert symbol.
 2. Change each AND gate to an invert-AND symbol.
- While making these conversions, **be vigilant about bubbles**.
- **Any bubble that is not compensated** by another bubble along the same line **needs an inverter, or the complementation of the input literal**.



NOR Implementation

- The transformation of the AND–OR diagram of Fig (a) into a NOR diagram is shown in the below Figure.
- The Boolean function for this circuit is

$$F = (AB + AB)(C + D)$$

  


 (a) AND–OR gates



NOR Implementation

- The equivalent **AND–OR** diagram can be **recognized from the NOR** diagram **by removing all the bubbles**.
- To compensate for the bubbles in four inputs, it is **necessary to complement the corresponding input literals**.



References

- Computer Organization and Architecture Designing for Performance Tenth Edition by William Stallings
- Digital Design With an Introduction to the Verilog HDL FIFTH EDITION by M Morris, M. and Michael, D., 2013.





OLLSCOIL NA GAILLIMHÉ
UNIVERSITY OF GALWAY

Thank *you*