



OLLSCOIL NA GAILLIMHĒ
UNIVERSITY OF GALWAY

CT101 Computing Systems

Dr. Bharathi Raja Chakravarthi

Lecturer-above-the-bar

Email: bharathi.raja@universityofgalway.ie



University
ofGalway.ie



OLLSCOIL NA GAILLIMHÉ
UNIVERSITY OF GALWAY

Revision

Introduction

- Digital circuits are frequently constructed with NAND or NOR gates rather than with AND and OR gates.
- NAND and NOR gates are easier to fabricate with electronic components and are the basic gates used in all IC digital logic families.
- Rules and procedures have been developed for the conversion from Boolean functions given in terms of **AND, OR, and NOT** into equivalent **NAND and NOR** logic diagrams.



Binary numbers and others

System	Radix	Allowable Digits
Binary	2	0 and 1
Octal	8	0, 1, 2, 3, 4, 5, 6, 7
Decimal	10	0, 1, 2, 3, 4, 5, 6, 7, 8, 9
Hexadecimal	16	0 to 9 A, B, C, D, E, F



Decimal to Binary

STEP 1

WHOLE NUMBER PART

- We convert the whole number and fractional parts separately and then combine the results.
- The whole number part of **85.375** is **85**. Divide this number repeatedly by **2** until the quotient becomes **0**.

		Remainders
2	85	1
2	42	0
2	21	1
2	10	0
2	5	1
2	2	0
2	1	1
	0	

Write the remainders
from bottom to top.

$$(85)_{10} = (1010101)_2$$



STEP 2

FRACTIONAL PART

The fractional part of **85.375** is **0.375**. Multiply the fractional part repeatedly by **2** until it becomes **0**.

- $0.375 \times 2 = 0.750$
- $0.750 \times 2 = 1.500$
- $0.500 \times 2 = 1.000$

STEP 3

From top to bottom, write the integer parts of the results to the fractional part of the number in base **2**.

$$(0.375)_{10} = (0.011)_2$$


Combine the whole number and fractional parts to obtain the overall result.

$$(85.375)_{10} = (1010101)_2 + (0.011)_2 = (1010101.011)_2$$



Binary to Decimal

(1010.11)₂

 

We multiply each binary digit with its place value and add the products.

$$(1010.11)_2 = (1 \times 2^3) + (0 \times 2^2) + (1 \times 2^1) + (0 \times 2^0) + (1 \times 2^{-1}) + (1 \times 2^{-2})$$

$$= 8 + 2 + \frac{1}{2} + \frac{1}{4}$$

$$= (10.75)_{10}$$



Decimal to Hexadecimal



Remainders	
16 479	F
16 29	D
16 1	1
0	

Write the remainders from **bottom to top**.

$$(479)_{10} = (1DF)_{16}$$



Hexadecimal to Decimal

  

$$(\mathbf{B65F})_{16} = (\mathbf{11} \times \mathbf{16^3}) + (\mathbf{6} \times \mathbf{16^2}) + (\mathbf{5} \times \mathbf{16^1}) + (\mathbf{15} \times \mathbf{16^0})$$

$$= 45056 + 1536 + 80 + 15$$

$$= (\mathbf{46687})_{10}$$



Decimal to Octal

Divide the number repeatedly by 8 until the quotient becomes 0.

$$(739)_{10}$$


	Remainders
8 739	3
8 92	4
8 11	3
8 1	1
0	

$$(739)_{10} = (1343)_8$$



Octal to Decimal

(137.24)₈

 

We multiply each digit with its place value and add the products.

$$(137.24)_8 = (1 \times 8^2) + (3 \times 8^1) + (7 \times 8^0) + (2 \times 8^{-1}) + (4 \times 8^{-2})$$

$$= 64 + 24 + 7 + \frac{2}{8} + \frac{4}{64}$$

$$= (95.3125)_{10}$$

$$(137.24)_8 = (95.3125)_{10}$$



Hexadecimal to Octal


Convert each hex digit to 4 binary digits and then convert each 3 binary digits to octal digits.

Example, we can take $(B65F)_{16}$

STEP 1

Hexadecimal to Binary

 
In the first step, we convert the hexadecimal number to binary.



STEP 2

Binary to Octal

 In the second step, we convert the binary number to octal.



Last STEP

Combining Results

Using the equalities we obtained in steps 1 and 2, we reach the following result.


$$(\mathbf{B65F})_{16} = (\mathbf{133137})_8$$



Hexadecimal to Binary

(A46.09)₁₆

 To convert a hexadecimal number to binary, we write 4 bit binary equivalent of each hexadecimal digit in the same order.



$$(A46.09)_{16} = (101001000110.00001001)_2$$



Homework

❑ Decimal to Hexadecimal

Example: Convert $(5386)_{10}$ to a hexadecimal $(?)_{16}$ number.

Number (Division)	Quotient	Remainder
5386 / 16	336	10 = A
336 / 16	21	0
21 / 16	1	5
1 / 16	0	1

Decimal Value → Hexadecimal Value


$(5386)_{10} \rightarrow (150A)_{16}$



Binary to Octal

(**1100.11011**)₂

 Starting from the binary point, we partition the binary number into groups of three bits.



In the **integer part**, we proceed to the left. To complete the leftmost group of bits, we append **two zeros** to the left.



In the **fractional part**, we proceed to the right. To complete the rightmost group of bits, we append **a zero** to the right.

$$(001)_2 = (1)_8$$

$$(100)_2 = (4)_8$$

$$(110)_2 = (6)_8$$

$$(110)_2 = (6)_8$$

We convert each group of binary numbers to octal and write them in the same order.


$$(1100.11011)_2 = (14.66)_8$$



Octal to Binary

(1743)₈

 To convert an octal number to binary, we write 3 bit binary equivalent of each octal digit in the same order.



$$(1743)_8 = (001111100011)_2$$




Octal to Hexadecimal

(46.1)₈

We can convert an octal number to hexadecimal in two steps.

STEP 1

 In the first step, we convert the octal number to binary.




To convert an octal number to binary, we write 3 bit binary equivalent of each octal digit in the same order.

$$(46.1)_8 = (100110.001)_2$$



STEP 2

 In the second step, we convert the binary number to hexadecimal.



Starting from the binary point, we partition the binary number into groups of 4 bits. In the whole number part, we proceed to the left and in the fractional part, we proceed to the right.

$$(100110.001)_2 = (26.2)_{16}$$

STEP 3

COMBINING RESULTS

Using the equalities we obtained in steps 1 and 2, we reach the following result.

$$(46.1)_8 = (26.2)_{16}$$



Diminished Radix Complement

- $(r - 1)$'s complement of N is $(r^n - 1) - N$

Where,

N - number

r - base

n - digits

- For decimal numbers,
 $r = 10$ and $r - 1 = 9$, 9's complement of N is

$$(10^n - 1) - N$$

- In this case, 10^n represents a number that consists of a single 1 followed by n 0's.

$10^n - 1$ is represented by n 9's



Radix Complement

- r 's complement of N is

$r^n - N$ for $N \neq 0$ and 0 for $N = 0$.

Where,

N - number

r - base

n - digits

- Radix complement is obtained **by adding 1** to the Diminished Radix Complement

$$r^n - N = [(r^n - 1) - N] + 1$$



Interpreting the Other Digits

Given n binary digits,

- the digit with **weight $2^{(n-1)}$ is the sign** and
- the digits with **weights $2^{(n-2)}$ down to 2^0 represents $2^{(n-1)}$** distinct elements.

There two popular ways to interpret the other digits:

1. Signed-Magnitude
2. Signed-Complement
 - a) Signed One's Complement
 - b) Signed Two's Complement



Signed-magnitude representation

01001 \longrightarrow 9 (unsigned) or +9 (signed)
↑
leftmost bit is 0 denoted positive

Positive


11001 \longrightarrow 25 (unsigned) or -9 (signed)
↗ ↘
leftmost bit is 1
denotes negative bits represent binary 9

Negative




Signed complement representation

 Signed 1's complement representation of -
9:



 Signed 2's complement representation of -
9:



Binary Logic

There are three basic logical operations: **AND, OR, and NOT**. Each operation produces a binary result, denoted by z .

- AND – represented by a **dot or absence** of an operator. **E.g.**, $x \cdot y = z$ or $xy = z$
- OR – represented by a **plus sign**. **E.g.**, $x + y = z$
- NOT – represented by a **prime** (sometimes by an overbar). **E.g.**, $x' = z$ or $\bar{x} = z$



Logic Gates

A logic gate is a simple switching circuit that determines whether an input pulse can pass through to the output in digital circuits.

(a) AND Gate:

Two-input AND gate




Truth Table

x	y	z
0	0	0
0	1	0
1	0	0
1	1	1



Logic Gates

Three-input AND gate

 


Truth Table

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1



Logic Gates

(b) OR Gate:

 


Truth Table

x	y	z
0	0	0
0	1	1
1	0	1
1	1	1



Logic Gates

Four-input OR gate

 

Truth Table


A	B	C	G
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1



Logic Gates

(c) NOT Gate:

NOT gate or inverter

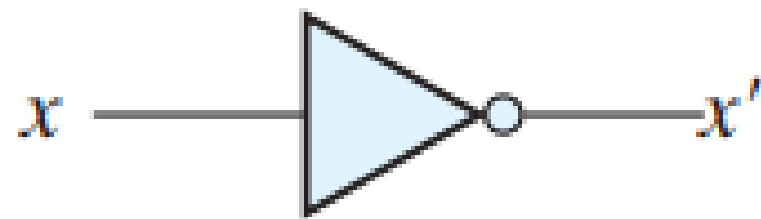

Truth Table.


NOT

x	x'
0	1
1	0



Logic Gates

Input – Output signals for gates

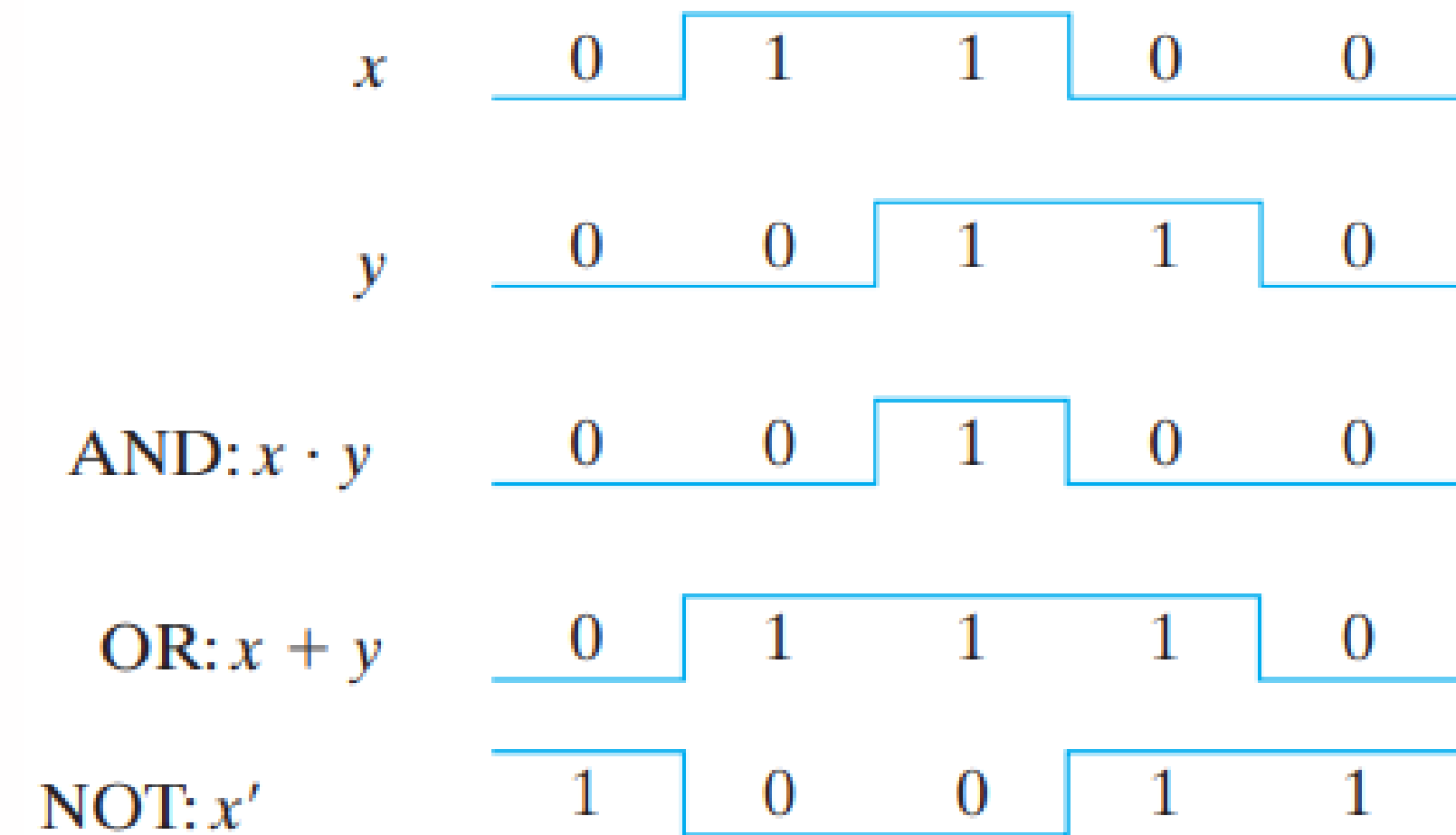

Operator Precedence

- The **operator precedence** for evaluating Boolean expressions is
 - (1) parentheses
 - (2) NOT
 - (3) AND
 - (4) OR
- **Expressions inside parentheses must be evaluated** before all other operations.
- The **next operation** that holds precedence is the **complement**, and **then follows the AND** and, **finally, the OR**.



Minterm/Standard product

The **2ⁿ different minterms** determined by a method shown in Table **for three variables**.

			Minterms		Maxterms	
x	y	z	Term	Designation	Term	Designation
0	0	0	$x'y'z'$	m_0	$x + y + z$	M_0
0	0	1	$x'y'z$	m_1	$x + y + z'$	M_1
0	1	0	$x'yz'$	m_2	$x + y' + z$	M_2
0	1	1	$x'yz$	m_3	$x + y' + z'$	M_3
1	0	0	$xy'z'$	m_4	$x' + y + z$	M_4
1	0	1	$xy'z$	m_5	$x' + y + z'$	M_5
1	1	0	xyz'	m_6	$x' + y' + z$	M_6
1	1	1	xyz	m_7	$x' + y' + z'$	M_7



Maxterm/Standard sum

The **eight(2ⁿ) maxterms for three variables**, together with their symbolic designations, are listed in Table.

Minterms					Maxterms	
x	y	z	Term	Designation	Term	Designation
0	0	0	$x'y'z'$	m_0	$x + y + z$	M_0
0	0	1	$x'y'z$	m_1	$x + y + z'$	M_1
0	1	0	$x'yz'$	m_2	$x + y' + z$	M_2
0	1	1	$x'yz$	m_3	$x + y' + z'$	M_3
1	0	0	$xy'z'$	m_4	$x' + y + z$	M_4
1	0	1	$xy'z$	m_5	$x' + y + z'$	M_5
1	1	0	xyz'	m_6	$x' + y' + z$	M_6
1	1	1	xyz	m_7	$x' + y' + z'$	M_7



Sum of Minterms

- Express the Boolean function $F = A + B'C$ as a sum of minterms.
- The function has three variables: A , B , and C . The first term A is missing two variables; therefore,

$$A = A(B + B') = AB + AB'$$

- This function is still missing one variable, so



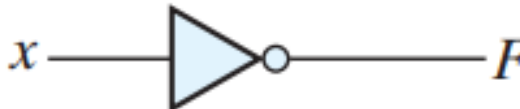

$$\begin{aligned} A &= AB(C + C') + AB'(C + C') \\ &= ABC + ABC' + AB'C + AB'C' \end{aligned}$$

- The second term $B'C$ is missing one variable; hence,

$$B'C = B'C(A + A') = AB'C + A'B'C$$







Digital Logic Gates

Name	Graphic symbol	Algebraic function	Truth table															
AND		$F = x \cdot y$	<table><tr><th>x</th><th>y</th><th>F</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	x	y	F	0	0	0	0	1	0	1	0	0	1	1	1
x	y	F																
0	0	0																
0	1	0																
1	0	0																
1	1	1																
OR		$F = x + y$	<table><tr><th>x</th><th>y</th><th>F</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	x	y	F	0	0	0	0	1	1	1	0	1	1	1	1
x	y	F																
0	0	0																
0	1	1																
1	0	1																
1	1	1																
Inverter		$F = x'$	<table><tr><th>x</th><th>F</th></tr><tr><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td></tr></table>	x	F	0	1	1	0									
x	F																	
0	1																	
1	0																	
Buffer		$F = x$	<table><tr><th>x</th><th>F</th></tr><tr><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td></tr></table>	x	F	0	0	1	1									
x	F																	
0	0																	
1	1																	




Digital Logic Gates

Name	Graphic symbol	Algebraic function	Truth table															
NAND		$F = (xy)'$	<table><tr><th>x</th><th>y</th><th>F</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	x	y	F	0	0	1	0	1	1	1	0	1	1	1	0
x	y	F																
0	0	1																
0	1	1																
1	0	1																
1	1	0																
NOR		$F = (x + y)'$	<table><tr><th>x</th><th>y</th><th>F</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	x	y	F	0	0	1	0	1	0	1	0	0	1	1	0
x	y	F																
0	0	1																
0	1	0																
1	0	0																
1	1	0																
Exclusive-OR (XOR)		$F = xy' + x'y$ $= x \oplus y$	<table><tr><th>x</th><th>y</th><th>F</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	x	y	F	0	0	0	0	1	1	1	0	1	1	1	0
x	y	F																
0	0	0																
0	1	1																
1	0	1																
1	1	0																
Exclusive-NOR or equivalence		$F = xy + x'y'$ $= (x \oplus y)'$	<table><tr><th>x</th><th>y</th><th>F</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	x	y	F	0	0	1	0	1	0	1	0	0	1	1	1
x	y	F																
0	0	1																
0	1	0																
1	0	0																
1	1	1																



Positive and Negative Logic

 - The graphic symbol for the negative-logic OR gate is shown in (f).



(f) Negative logic OR gate

- The small triangles in the inputs and output designate a **polarity indicator**, the presence of which along a terminal signifies that negative logic is assumed for the signal.
- Thus, the same physical gate can operate either as a positive-logic AND gate or as a negative-logic OR gate.




K-map

- A K-map is a diagram made up of squares, with each square **representing one minterm of the function that is to be minimized.**
- The map **presents a visual diagram of all possible ways** a function may be expressed in standard form.
- The simplified expressions produced by the map are always in one of the **two standard forms**:
 - sum of products or
 - products of sums



Two-Variable K-Map

 - The two-variable map is shown here.
- Four minterms for two variables.
- (b) shows the relationship between the squares and the two variables x and y .
- **0** and **1** designate the values of variables.
- Variable x appears primed in row 0 and unprimed in row 1.
- Similarly, y appears primed in column 0 and unprimed in column 1.



Two-Variable K-Map

- The two-variable map becomes **another useful way to represent any one of the 16 Boolean functions of two variables.**
- Example, the function xy is shown Fig. (a).

		y	
		0	1
x	0	m_0	m_1
	1	m_2	m_3


(a) xy

		y	
		0	1
x	0	m_0	m_1
	1	m_2	m_3

(b) $x + y$



Two-Variable K-Map

 

- Since $\mathbf{xy} = \mathbf{m_3}$, 1 is placed inside the square m_3 .
- $\mathbf{x + y}$ function is represented in the map of Fig. (b) by three squares marked with 1's.
- These squares are found from the minterms of the function:

$$\mathbf{m_1 + m_2 + m_3 = x'y + xy' + xy = x + y}$$



Three-Variable K-Map

- A three-variable K-map is shown here.

m_0	m_1	m_3	m_2
m_4	m_5	m_7	m_6

(a)

		y			
		00	01	11	10
x	0	m_0 $x'y'z'$	m_1 $x'y'z$	m_3 $x'yz$	m_2 $x'yz'$
	1	m_4 $xy'z'$	m_5 $xy'z$	m_7 xyz	m_6 xyz'
		z			

(b)

- Eight minterms for three binary variables; the map consists of eight squares.
- Only one bit changes in value from one adjacent column to the next.



Three-Variable K-Map

m_0	m_1	m_3	m_2
m_4	m_5	m_7	m_6

(a)

		y				
		yz		00	01	11
x	0	m_0	m_1	m_3	m_2	
		$x'y'z'$	$x'y'z$	$x'yz$	$x'yz'$	
x	1	m_4	m_5	m_7	m_6	
		$xy'z'$	$xy'z$	xyz	xyz'	
		z				

(b)

- The map drawn in part (b) is marked with numbers in each row and each column to show the relationship between the squares and the three variables.
- For example, the square assigned to m_5 :
row - 1 and column - 01.
- When these two numbers are concatenated, they give the binary number **101**, whose decimal equivalent is **5**.



Four-Variable K-Map

- A map for Boolean functions with four binary variables (w, x, y, z) is presented in Figure.

m_0	m_1	m_3	m_2
m_4	m_5	m_7	m_6
m_{12}	m_{13}	m_{15}	m_{14}
m_8	m_9	m_{11}	m_{10}

(a)

$wx \backslash yz$		y			
		00	01	11	10
w	00	m_0 $w'x'y'z'$	m_1 $w'x'y'z$	m_3 $w'x'yz$	m_2 $w'x'yz'$
	01	m_4 $w'xy'z'$	m_5 $w'xy'z$	m_7 $w'xyz$	m_6 $w'xyz'$
	11	m_{12} $wxy'z'$	m_{13} $wxy'z$	m_{15} $wxyz$	m_{14} $wxyz'$
	10	m_8 $wx'y'z'$	m_9 $wx'y'z$	m_{11} $wx'yz$	m_{10} $wx'yz'$

(b)



The 16 minterms are listed along with the squares assigned to each.

Illustrate the relationship between squares and the four variables.




NAND Circuits

  - To facilitate the conversion to NAND logic, defining an **alternative graphic symbol** for the **gate** is convenient.
- **Two equivalent graphic symbols** for the NAND gate are shown in Figure.




NAND Circuits

 

 (a) AND-invert

- The **AND-invert symbol** has been defined previously and consists of an AND graphic symbol followed by a small circle negation indicator referred to as a bubble.



(b) Invert-OR

- The **invert-OR symbol** for the NAND gate follows DeMorgan's theorem and the convention that the negation indicator (bubble) denotes complementation.
- The two graphic symbols' representations are useful in analyzing and designing NAND circuits.
- When both symbols are mixed in the same diagram, the circuit is said to be in mixed notation.





NOR Implementation

- The **NOR** operation is the **dual of the NAND** operation.
- Therefore, all procedures and **rules for NOR logic** are the **duals of the corresponding procedures and rules developed for NAND logic**.
- The NOR gate is another universal gate that can be used to implement any Boolean function.



NOR Implementation

  
- The **implementation of the complement, OR, and AND operations with NOR** gates is shown in Figure below.
- The complement operation is obtained from a **one input NOR gate that behaves exactly like an inverter**.
- The **OR operation requires two NOR gates**, and the **AND operation is obtained with a NOR gate that has inverters in each input**.



NOR Implementation


Two graphic symbols for the mixed notation:

 - The OR-invert symbol defines the **NOR operation as an OR followed by a complement**.



 (a) OR-invert

- The invert-AND symbol **complements each input and then performs an AND operation**.



(b) Invert-AND

- The two symbols designate the same NOR operation and are logically identical **because of DeMorgan's theorem**.



References

- Computer Organization and Architecture Designing for Performance Tenth Edition by William Stallings
- Digital Design With an Introduction to the Verilog HDL FIFTH EDITION by M Morris, M. and Michael, D., 2013.





OLLSCOIL NA GAILLIMHÉ
UNIVERSITY OF GALWAY

Thank *you*